
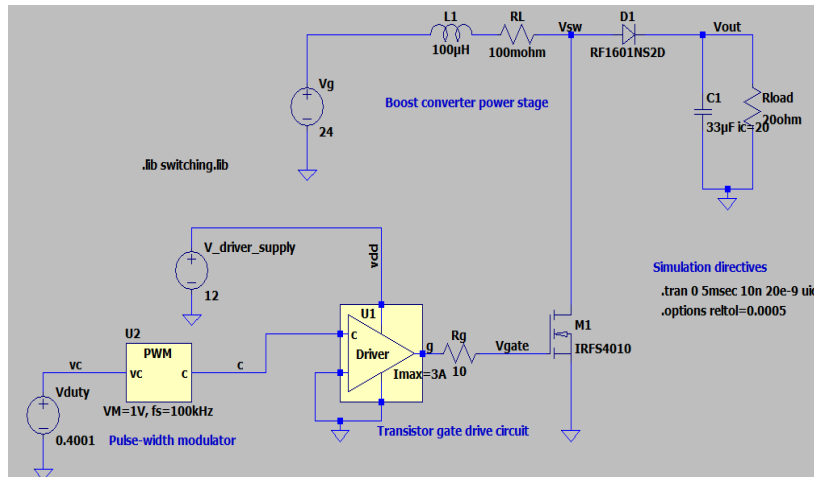


# Week 1

## Introduction to Power Electronics

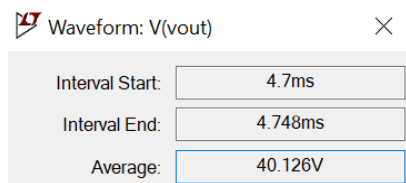


What is the steady-state average output voltage (expressed in volts)?



$$V_{out} = 40.126;$$

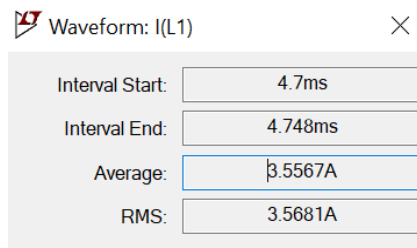
What is the steady-state average inductor current (in amps)?



$$i_L = 3.55;$$

What is the steady-state output power (in watts)?

$$P_{out} = I(R_{load}) * V(v_{out})$$

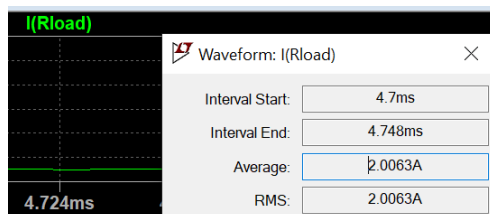

$$i_R = 2.0063;$$

$$P_{out} = i_L V_{out}$$

$$P_{out} = 80.5048$$

**What is the average power drawn out of the input source  $V_g$  during steady-state operation of the converter (in watts)?**


$$P_{in} = V_g i_L$$

$$V_g = 24;$$

$$P_{in} = V_g i_L$$

$$P_{in} = 85.2000$$

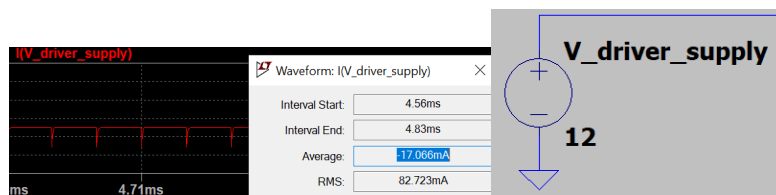**What is the average power consumption of the gate driver (in watts)?**



$$i_{driver} = 17.066e-3;$$

% Probe is in negative direction.

$$V_{dd} = 12;$$

$$P_{gatedriver} = i_{driver} V_{dd}$$

$$P_{gatedriver} = 0.2048$$

**What is the converter efficiency (enter a numeric value between 0 and 1)?**

$$eff = P_{out} / P_{in}$$

$$eff = 0.9449$$

% According to grader;  $eff = 0.946 - 0.948$

**Now change the control voltage input to the pulse-width modulator, so that it produces a control signal having a duty cycle of 0.6. Run the simulation again. What is the new steady-state average output voltage?**

$$ans = 60$$